

Different Circuit Elements



(1) Resistance (R)

↳ Opposition offered by a substance to the flow of current in a circuit is called its resistance.

- A wire is said to have a resistance of 1Ω when a potential difference of $1V$ across it causes a current of $1A$ in it.

↳ Factors on which the resistance depends:-

a) Temperature ($T \uparrow, R \uparrow$)

b) Length of a conductor (l)

c) Cross-sectional area ($A \uparrow, R \downarrow$)

d) Specific Resistance / Resistivity (ρ)

- Specific resistance is the resistance of the material with length(l) of $1m$ & area of cross-section (A) of $1 m^2$.

$$\Rightarrow R = \frac{\rho l}{A}$$

(2) Conductance (G)

$$G = \frac{1}{R}$$

∴ Unit is ohm^{-1} @ mho @ siemens.

↳ Resistance in Series

$$V = V_1 + V_2 + V_3$$

$$\Rightarrow IR_{\text{eq}} = IR_1 + IR_2 + IR_3$$

$$\therefore \boxed{R_{\text{eq}} = R_1 + R_2 + R_3}$$

~~↳~~ Voltage Divider Rule

$$V_1 = \frac{VR_1}{R_1 + R_2 + R_3} ; V_2 = \frac{VR_2}{R_1 + R_2 + R_3} ; V_3 = \frac{VR_3}{R_1 + R_2 + R_3}$$

↳ Resistance in Parallel

$$\frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

~~↳~~ Current Divider Rule

$$I_1 = I \frac{R_1}{R_1 + R_2} \quad \& \quad I_2 = I \frac{R_2}{R_1 + R_2}$$

Capacitor


Two conducting plates separated by a dielectric medium to store charge is called a capacitor.

& Capacitance → It is the ability to store charge inside a capacitor.

Unit → Farad (F)


Symbol →

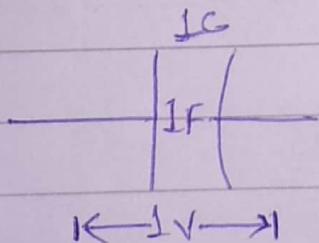↪ A capacitor is said to have capacitance of 1F if a charge of 1C accumulate on each plate when a potential difference of 1V is applied across it.



Capacitance in series
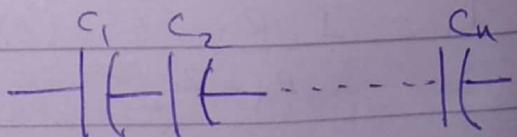
$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$



Capacitance in parallel

$$C_p = C_1 + C_2 + C_3 + \dots + C_n$$

Inductor

It consists of a large number of turns having either a ferromagnetic core or air core.

& Inductance → It is the property of an inductor that opposes any sudden change in the amount of current flowing.

In series

$$L_T = L_1 + L_2 + L_3 + \dots + L_n$$

In parallel

Laws:-

OHM's Law

"The ratio of the potential difference across the ends of a conductor to the current flowing in it is constant provided the physical conditions should not change."


Kirchoff's law

(i) Kirchoff's Current Law

The Algebraic sum of a current flowing towards a junction in an electric circuit is 0 (zero).




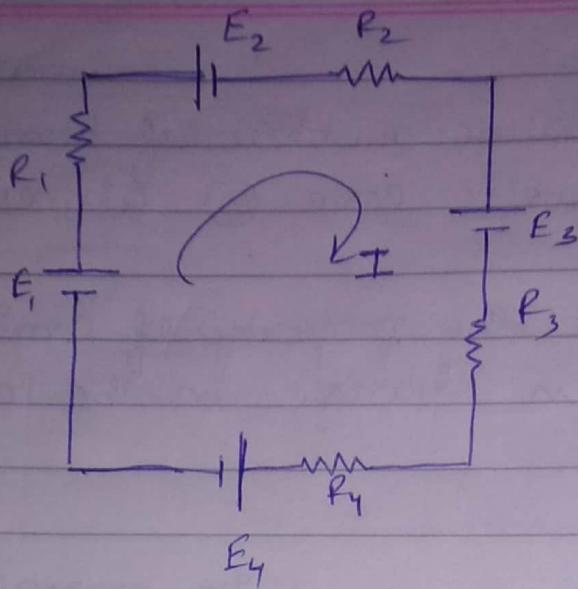
(ii) Kirchoff's Voltage Law

In a closed mesh or loop, the algebraic sum of all the emfs & the voltage drops is equal to zero (0),



~~V.V.Imp~~


Sign convention

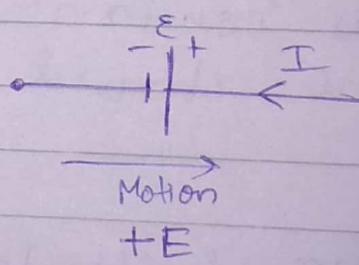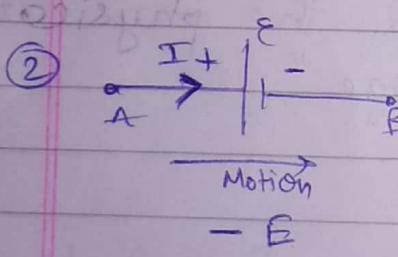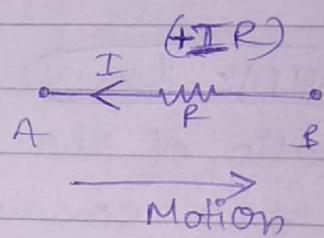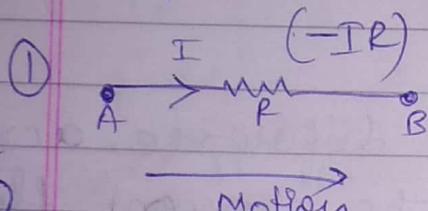


~~defn.~~ **★ Ideal voltage source** → It is that ~~voltage~~ voltage source, its output remains constant whatever be the load connected.

★ Ideal Current Source → It is that current source, whose internal resistance is infinite so that it supplies constant current in the loop.

SOURCE CONVERSION

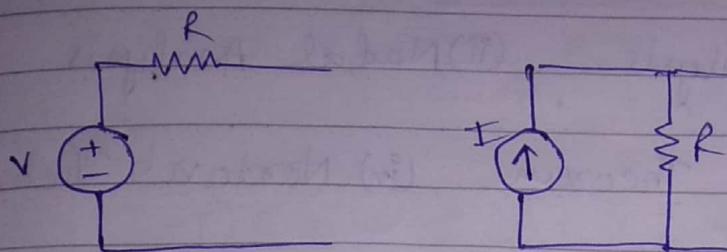


$$I = \frac{V}{R}$$

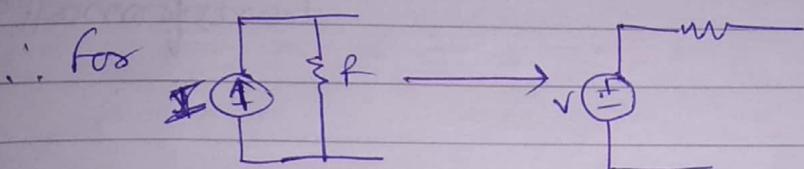

for $V = IR$

E.g. A voltage source with a series resistance can be converted into an equivalent current source with parallel ~~series~~ resistance & vice versa.


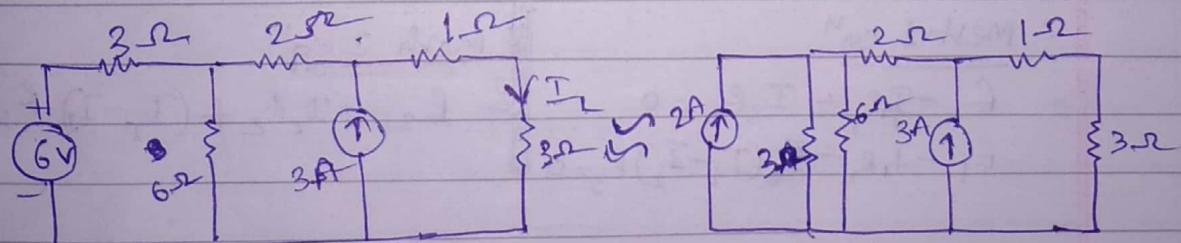
Q) Using source conversion find the current I_L .





$$\frac{1}{R_{eq}} = \frac{1}{2} + \frac{1}{3} = \frac{5}{6}$$

$$R_{eq} = \frac{6}{5} \Omega$$

$$I_L = \frac{V}{R_{eq}}$$

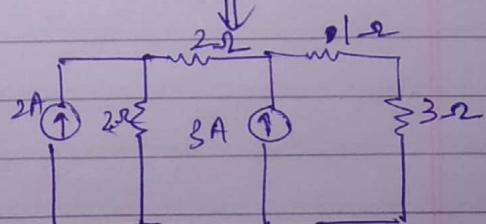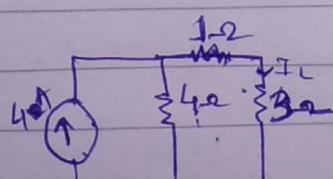


$$I_L = 2 \text{ A}$$

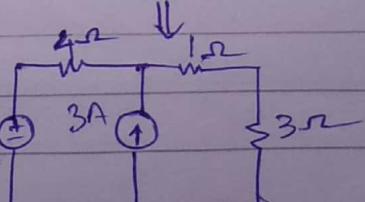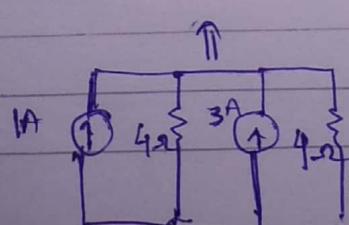


★ Analysis of Electric circuit

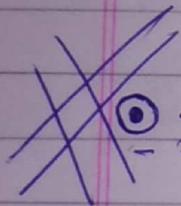- (i) Mesh Analysis
- (ii) Nodal Analysis
- (iii) Thevenin's Theorem
- (iv) Norton's Theorem
- (v) Superposition Theorem
- (vi) Star-delta & delta-star transformation



Mesh Analysis :-

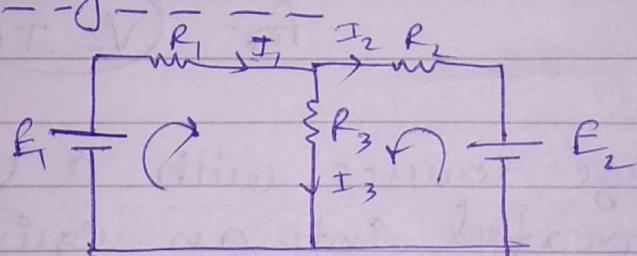

$$I_3 \rightarrow I_1 - I_2$$

Steps 1

1) Find the no. of mesh

2) Write mesh eqn's by using KVL

∴ Mesh 1 eqn

$$E_1 - I_1 R_1 - I_3 R_3 = 0$$

$$E_1 - I_1 R_1 - (I_1 - I_2) R_3 = 0$$


Mesh 2 eqn

$$E_2 + I_2 R_2 + (I_2 - I_1) R_3 = 0$$

Mesh-1

$$E_1 = I_1 R_1 + (I_1 - I_3) R_3 + \cancel{(I_1 - I_2) R_2} \quad \text{--- } ①$$
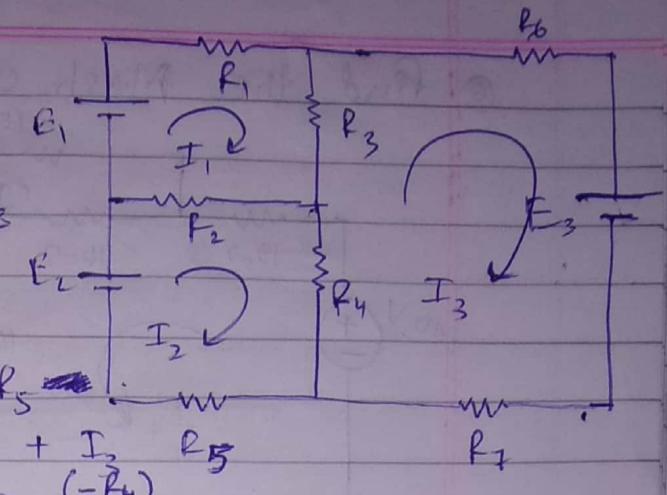
$$= I_1 (R_1 + R_3) - I_2 R_2 - R_3 I_3$$



Mesh-2

$$E_2 = (I_2 - I_1) R_2 + (I_2 - I_3) R_4 + \cancel{I_2 R_5} \quad \text{--- } ②$$

$$= I_2 (-R_2) + I_2 (R_2 + R_4 + R_5) + \cancel{I_2 (-R_4)} R_5$$

Mesh-3

$$\bullet E_3 = -I_3 R_7 - (I_3 - I_2) R_4 - (I_3 - I_1) R_3 - \cancel{I_3 R_6}$$

$$-E_3 = \bullet I_1 (\bullet R_3) + I_2 (\bullet R_4) + I_3 (-R_7 - R_4 - R_3 - R_6) \quad \text{--- } ③$$

Here

R_1 = Self resistance of
Mesh-1

R_2 = Self resistance of
Mesh-2


$$\therefore \begin{bmatrix} R_{11} & R_{12} & R_{13} \\ R_{21} & R_{22} & R_{23} \\ R_{31} & R_{32} & R_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} E_1 \\ E_2 \\ E_3 \end{bmatrix}$$

$$\& R_{12} = R_{21}$$

$$R_{23} = R_{32}$$

$$I_1 = \frac{\Delta_1}{\Delta} \quad \& I_2 = \frac{\Delta_2}{\Delta} \leftarrow I_3 \cancel{\frac{\Delta_3}{\Delta}}$$

① Find the Mesh currents I_1, I_2, I_3

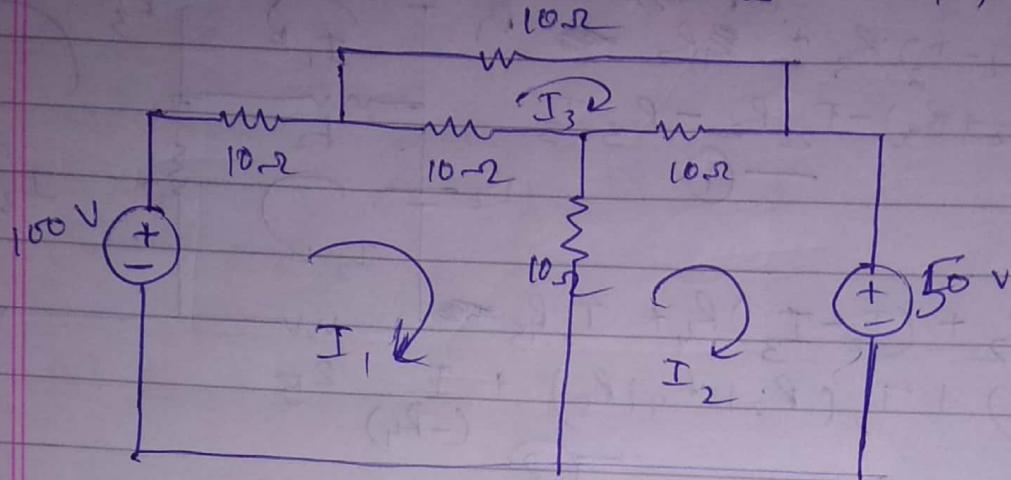

Mesh 1

$$100 - I_1(10) - (I_1 - I_3)10 - (I_1 - I_2)10 = 0$$

$$\Rightarrow I_1(-30) + I_2(10) + I_3(10) = -100$$

$$\Rightarrow 30I_1 - 10I_2 - 10I_3 = 100$$

Mesh 2


$$-50 - (I_2 - I_1)10 - (I_2 - I_3)10 = 0$$

$$+ 10I_1$$

Mesh 3

$$-10I_3 - (I_3 - I_1)10 - (I_3 - I_2)10 = 0$$

~~X~~ Nodal Analysis

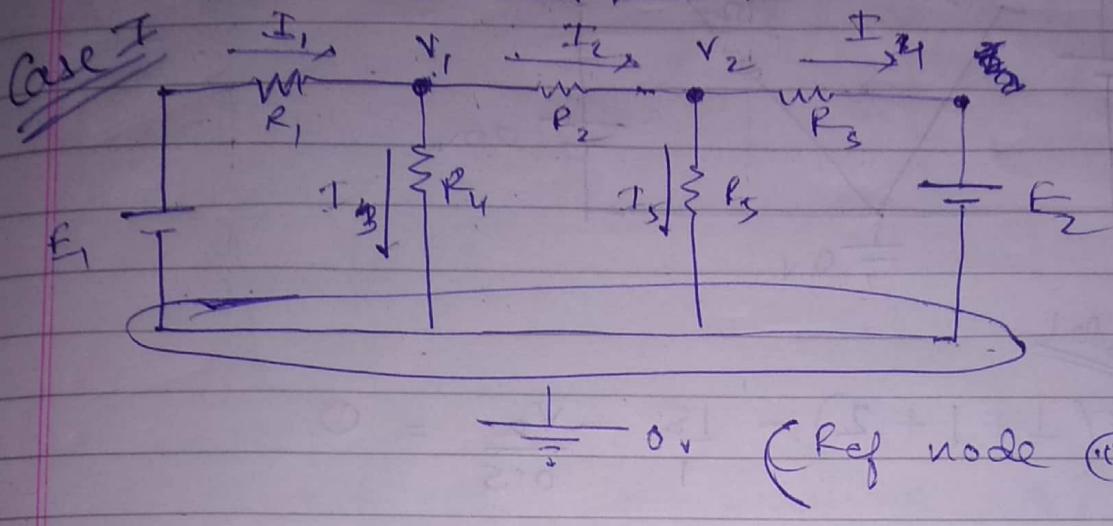

At node 1

$$I_1 = I_2 + I_3 \rightarrow \textcircled{1} I_1 = \frac{E_1 - V_1}{R_1}; I_3 = \frac{V_1 - 0}{R_4}$$

$$\textcircled{2} I_2 = \frac{V_1 - V_2}{R_2}$$


$$\therefore V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_4} \right) - \frac{V_2}{R_2} = \frac{E_1}{R_1} \textcircled{2}$$

At node 2

$$I_2 = I_5 + I_4; I_2 = \frac{V_1 - V_2}{R_2}; I_4 = \frac{V_2 - 0}{R_3} \textcircled{3}$$

$$I_5 = \frac{V_2 - 0}{R_5} = \frac{V_2}{R_5}$$
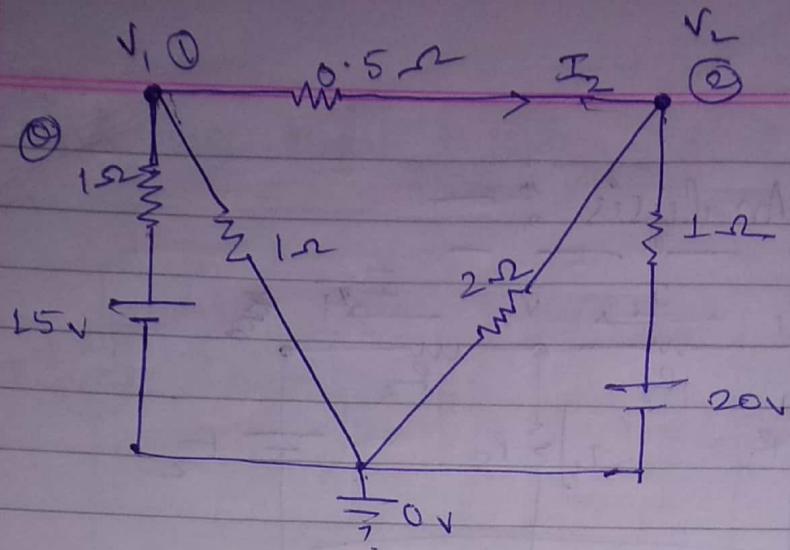
$$\therefore V_2 \left(\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_5} \right) - \frac{V_1}{R_2} - \frac{E_2}{R_3} = 0 \textcircled{4}$$



At node 1

$$V_1 \left(\frac{1}{1} + \frac{1}{0.5} + \frac{1}{2} \right) - \frac{15}{1} - \frac{V_2}{0.5} = 0$$

~~$$4V_1 - 2V_2 = 15$$~~

At node 2

$$V_2 \left(\frac{1}{1} + \frac{1}{0.5} + \frac{1}{2} \right) - \frac{V_1}{0.5} - \frac{20}{1} = 0$$

$$(3.5)V_2 - 2V_1 = 20$$

$$-2V_1 + (3.5)V_2 = 20 \quad \times 2$$

~~$$6V_1 - 4V_2 - 6V_2 + 10.5V_2 = 90$$

$$V_1 = \frac{90}{6.5} = 13.8 \text{ V}$$~~

~~$$3V_1 - 2V_2 - 4V_1 + 7V_2 = 15 + 40$$

$$5V_2 = 55$$

$$V_2 = 11 \text{ V}$$~~


$$4(V_1) - 2(11) = 15$$

$$V_1 = \frac{37}{4} \text{ V}$$

Nodal Analysis :-

Case - II

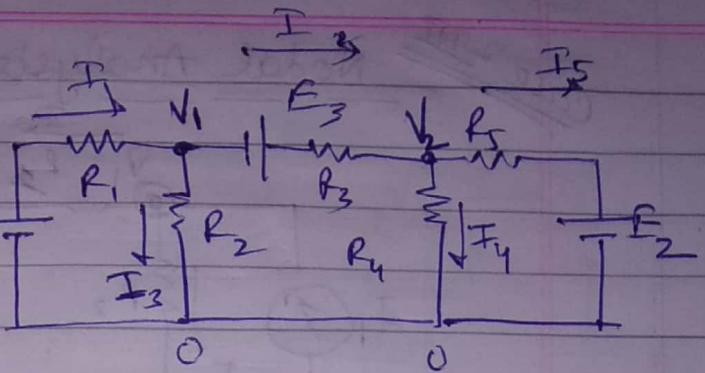When a battery is present in b/w 2 nodes.



At node - 1

$$I_1 = I_3 + I_2$$

$$I_1 = \frac{E_1 - V_1}{R_1} ; I_3 = \frac{V_1 - 0}{R_2} ; I_2 = \frac{V_1 + E_3 - V_2}{R_3}$$

$$V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) - \frac{E_1}{R_1} + \frac{E_3}{R_3} - \frac{V_2}{R_3} = 0$$


At node - 2

$$I_2 = I_4 + I_5$$

$$I_2 = \frac{V_1 + E_3 - V_2}{R_3} ; I_4 = \frac{V_2 - 0}{R_4} ; I_5 = \frac{V_2 - E_2}{R_5}$$

$$V_2 \left(\frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} \right) - \frac{V_1}{R_3} - \frac{E_2}{R_4} - \frac{E_3}{R_5} = 0$$

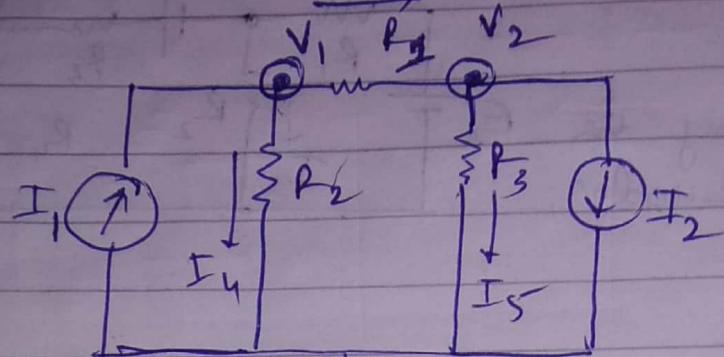Case III Nodal Analysis with coincident sources



At node 1

$$I_1 = I_4 + I_3 \quad \text{--- (1)}$$

$$I_4 = \frac{V_1 - 0}{R_2} = \frac{V_1}{R_2}$$

$$+ I_3 = \frac{V_1 - V_2}{R_1}$$

$$I_1 = \frac{V_1}{R_2} + \frac{V_1 - V_2}{R_1}$$

$$= V_1 \left(\frac{1}{R_2} + \frac{1}{R_1} \right) - \frac{V_2}{R_1} \quad \text{--- (2)}$$


At node 2

$$I_3 = I_2 + I_5 \quad \text{--- (3)}$$

$$I_3 = \frac{V_1 - V_2}{R_1}; I_5 = \frac{V_2 - 0}{R_3}$$

$$V_2 \left(\frac{1}{R_1} + \frac{1}{R_3} \right) - \frac{V_1}{R_1} = -I_2 \quad \text{--- (4)}$$

⑨ Write the node equations.

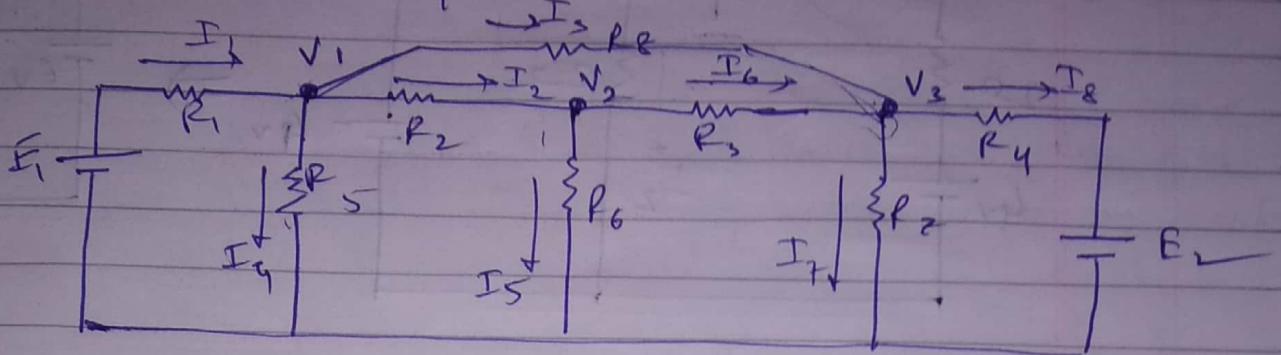

At node 1

$$V_1 \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_5} \right) - \frac{E_1}{R_1} - \frac{V_2}{R_2} - \frac{V_3}{R_8} = 0$$

$$+ \frac{1}{R_8}$$

At node 2


~~$$V_2 \left(\frac{1}{R_2} + \frac{1}{R_6} + \frac{1}{R_3} \right) - \frac{V_1}{R_2} - \frac{V_3}{R_3} = 0$$~~

At node 3

~~$$V_3 \left(\frac{1}{R_3} + \frac{1}{R_8} + \frac{1}{R_7} + \frac{1}{R_4} \right) - \frac{E_2}{R_4} - \frac{V_2}{R_3} - \frac{V_1}{R_8} = 0$$~~

~~B~~ ~~$I_8 = I_7 + I_6$~~

$$I_3 + I_6 = I_7 + I_8$$

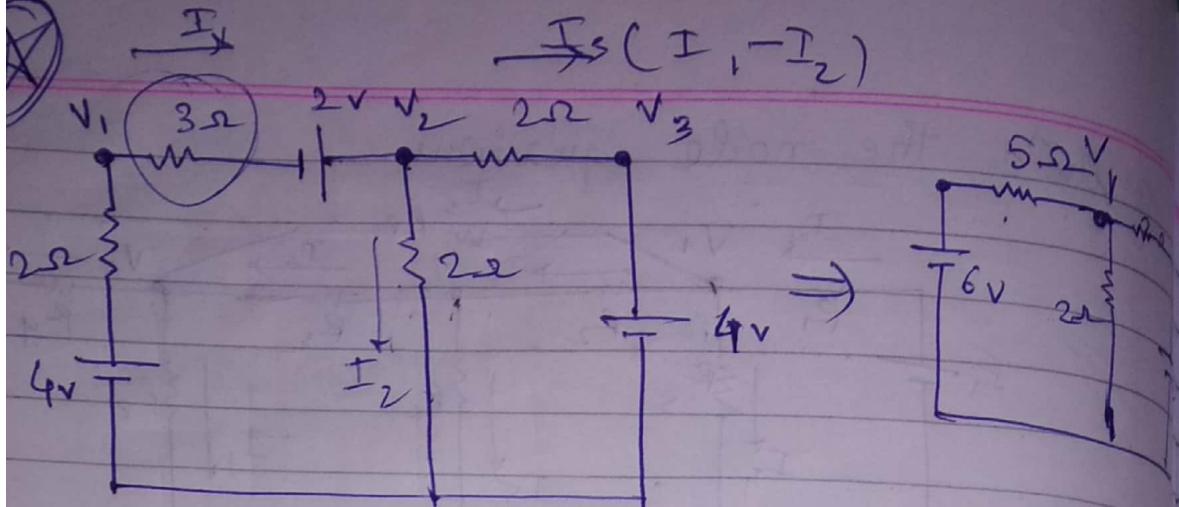

$$I_1 = I_2 + I_3$$

~~$$V_1 + V_2 - V_3 = \frac{V}{2} + \dots$$~~

~~$$I_1 = I_2 + I_3$$~~

~~$$(V_1 + V_2) + \frac{2}{3}V_3 - V_2 = 0$$~~

$$V_1 \left(\frac{1}{5} + \frac{1}{2} + \frac{1}{2} \right) - \frac{4+2}{5} - \frac{4}{2}$$


$$V_1 = 8$$

$$I_{3,2} = 0.67A$$


V.I.M.S


① Superposition Theorem

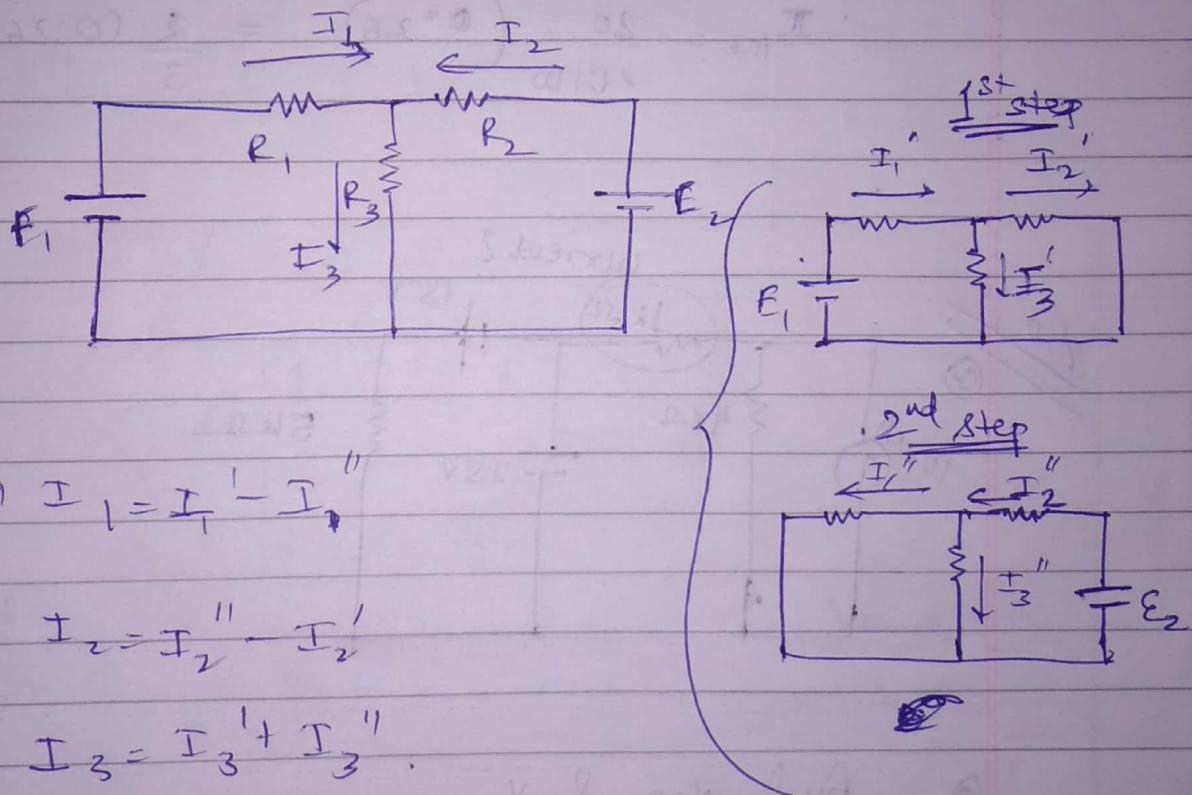In a network containing more than one source of emf, the current which flows at any time is the sum of all the currents which would flow at that point if each emf sources were considered separately & all other emf source replaced for the time being, by resistances equal to their internal resistance.



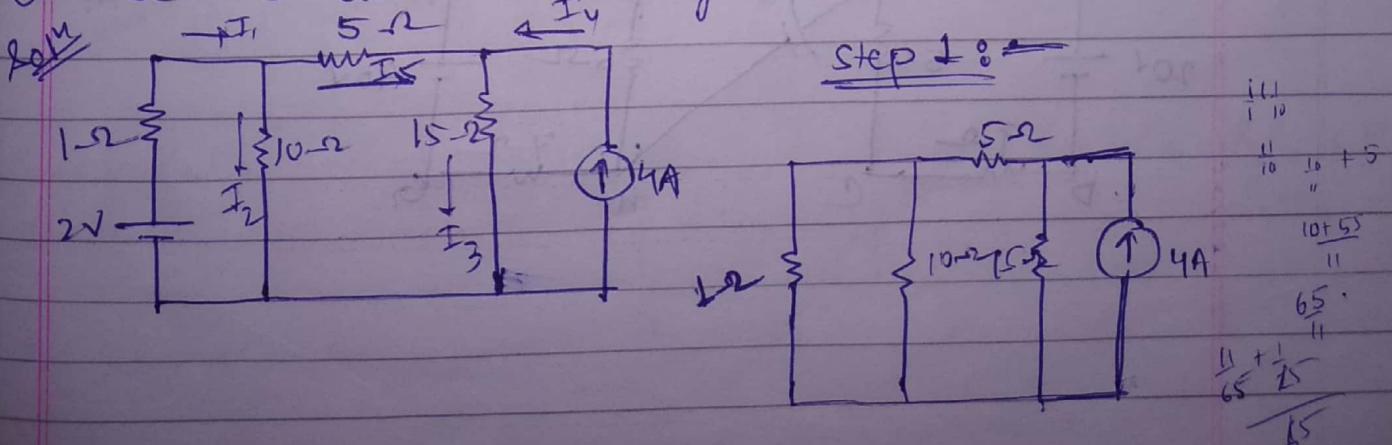
② Find the current through $10\ \Omega$ shunt.



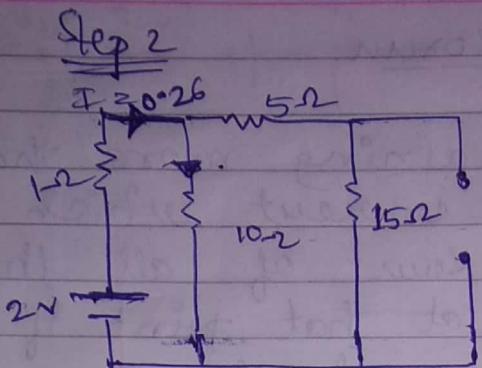


$$R_{eq} = \frac{23}{3} \quad \text{&} \quad I = \frac{2}{\frac{23}{3}} = 0.26 \text{ A}$$


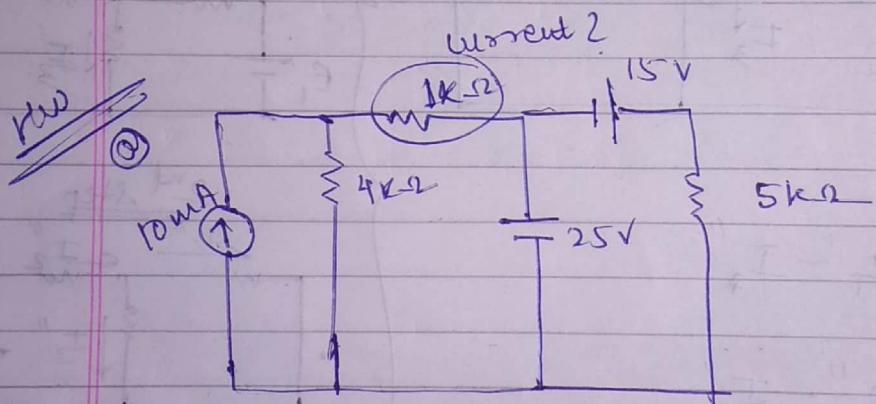
$$\therefore I_{10\Omega} = \frac{20}{20+10} (0.26) = \frac{2}{3} (0.26) = 0.08666 \text{ A} \\ = 0.1732$$




② find V_{CE} & V_{AO}

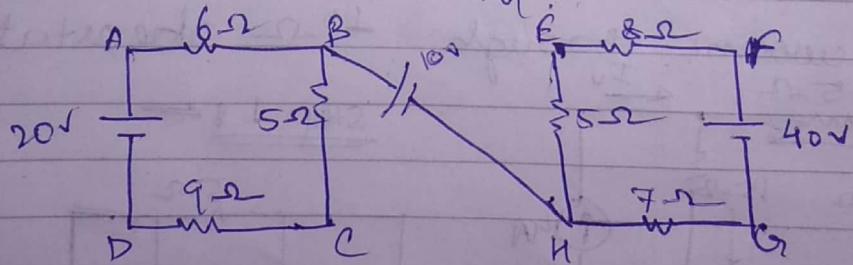

* Thevenin's Theorem

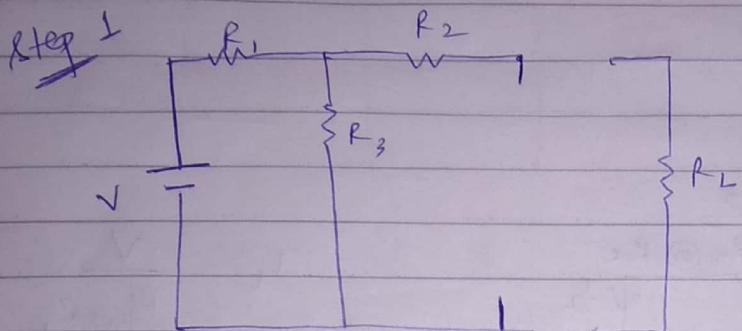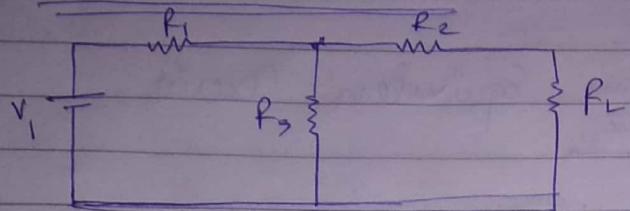

Step 2 Find V_{th} or V_{oc}

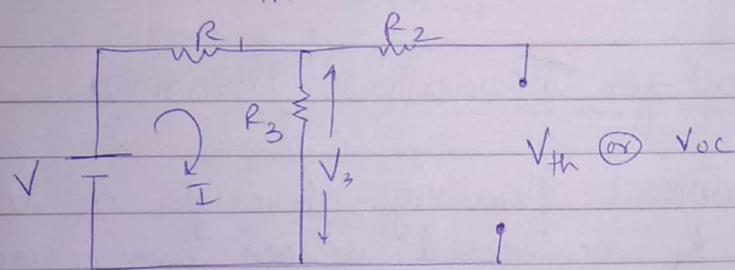


$$\therefore V_{th} \text{ or } V_{oc} = V_3$$

$$\Rightarrow I = \frac{V}{R_1 + R_3}$$

$$\Rightarrow V_{th} = I R_3$$


& get V_{th} .

Step 3 Find R_{th}

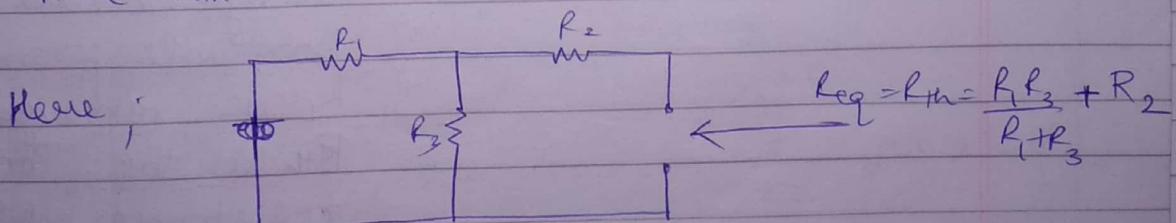


Step IV

Draw thevenin's equivalent circuit.

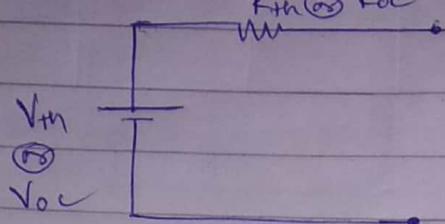

Step V

Insert R_L

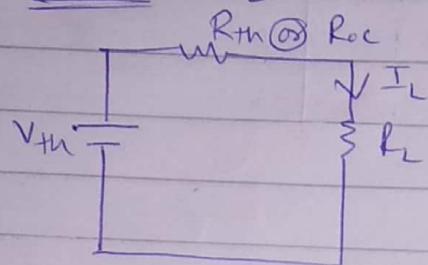

$$I_L = \frac{V}{R_{th} + R_L}$$

→ Statement for Thevenin's Theorem

"The current flowing through a load resistance R_L connected across any two terminals 'A' & 'B' of a linear active network is given by



$$I_L = \frac{V_{th}}{R_{th} + R_L}; \text{ where}$$

→ V_{th} or $V_{oc} \Rightarrow$ open circuit voltage across the 2 terminals from which R_L is removed and R_{th} is the Thevenin's resistance which is the resistance of the network as viewed back into the terminals 'A' & 'B' with all

open circuited network from

voltage source replaced by their internal resistance.

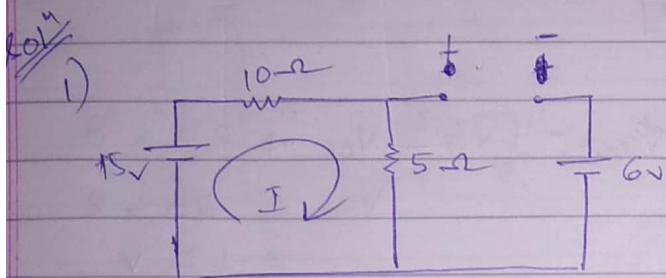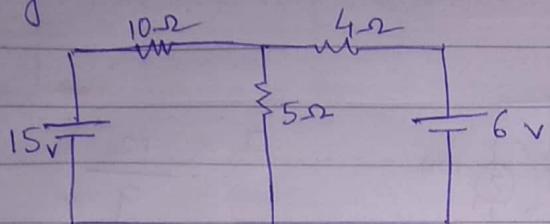- ② Find the current in 4 ohm resistance by using Thevenin's Theorem.




$$V_{th} + 6 = 0.5$$

$$-V_{oc} - 6 = -5$$


$$\frac{15}{15} = 1 \text{ A}$$

$$\Rightarrow V_{oc} = -1 \text{ V}$$

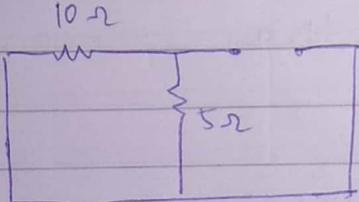



$$R_{th} = \frac{50}{15} = \frac{10}{3} \Omega$$

∴ Thevenin's Equivalent Circuit

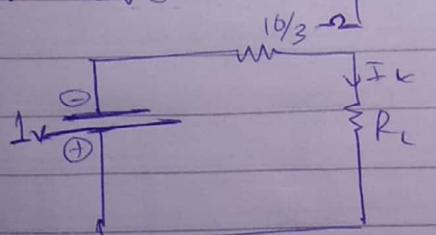

$$I_L = \frac{-1}{\frac{16}{3} + 4} = -\frac{3}{22} = -0.136 \text{ A}$$


Q) Find current in 4Ω resistor.

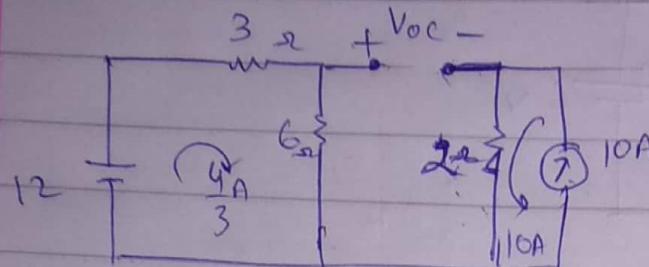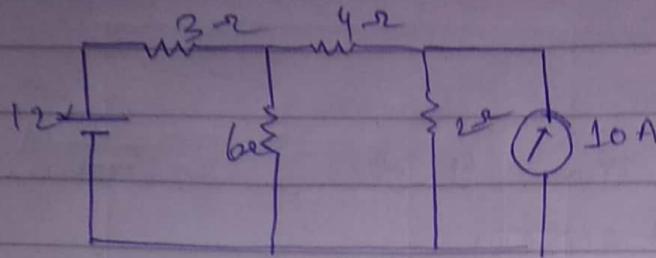


$$I = \frac{12}{9} = \frac{4}{3} A$$

~~$$V_{oc} - \frac{4}{3} \times 6^2 = V_{oc} + 20 = 0$$~~

$$V_{oc} = 20 - 8 \\ \approx 12 V$$

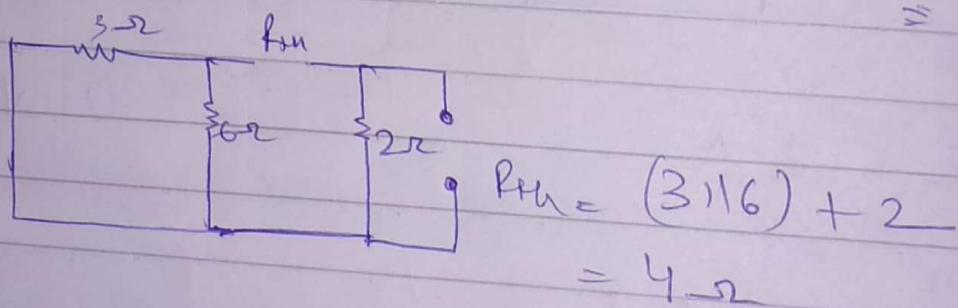


\therefore Thevenin's equivalent circuit

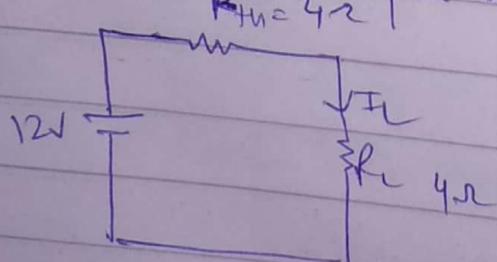


$$I_L = \frac{12}{8} = \frac{3}{2} = 1.5 A$$

Q) Find the current in 10Ω resistor.


By superposition thm.

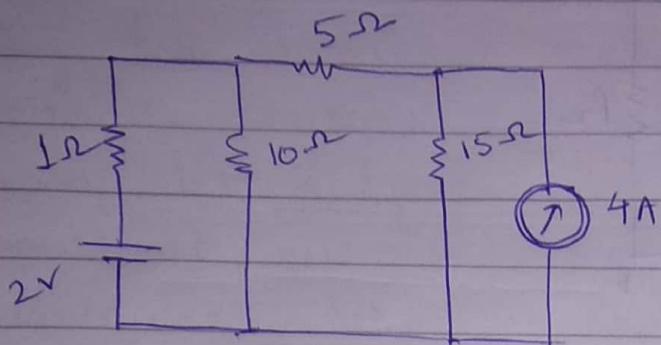


Q)

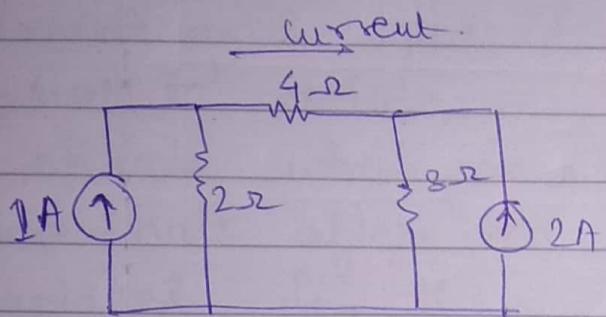

~~N.Imp~~
★ Norton's Theorem

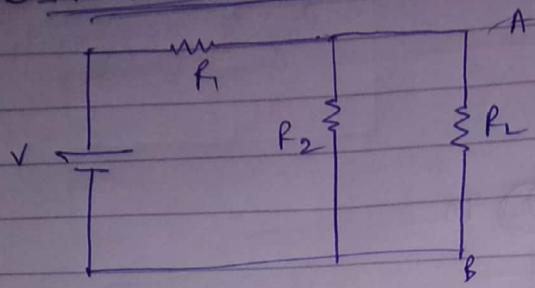


Step ①
Remove R_L

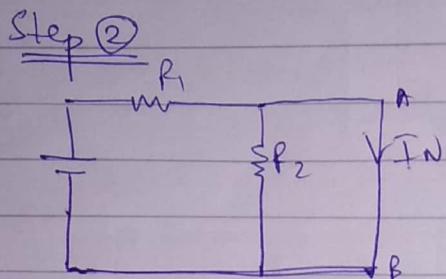


Step ②

find I_{IN} or I_{SC} $I_N = \frac{V}{R_1}$


Step ③
Find $R_N = R_{th}$

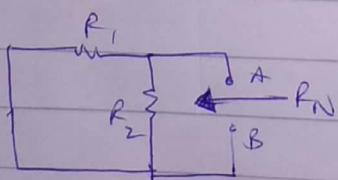

Step ④

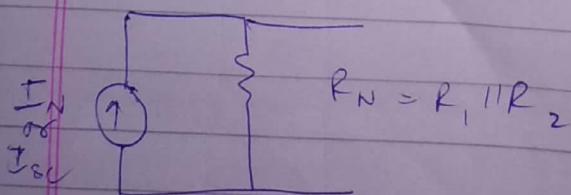

Step ⑤

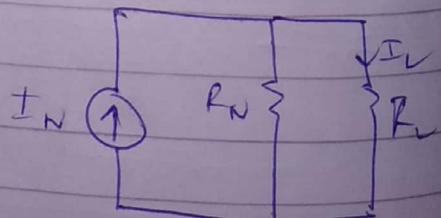


$$I_L = I_N \times \frac{R_N}{R_L + R_N}$$


Statement

"Any two terminal active network containing voltage sources & resistances when viewed from its output terminals is equivalent to a constant current source with a parallel resistance. The constant current is equal to the current which would flow in a short circuit path placed across the terminals & parallel resistance is the resistance of the network when viewed from these open circuited terminals after all voltage & current sources replaced by their internal resistance".

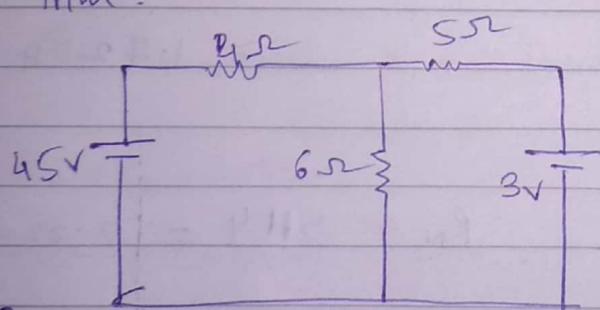② find current in 6Ω resistor using Norton's Thm.



The V_{oc}

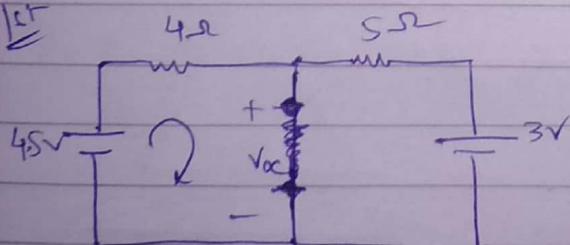

$$4.5 - 4I - 5I - 3 = 0$$

$$9I = 4.5$$


$$I = \frac{4.5}{9} = 0.167$$

$$\therefore 45 - 4 \times 0.167 - V_{oc} = 0$$


$$V_{oc} = 4.5 - 4 \times 0.167$$

$$= 4.5 - 0.668$$

$$= 3.832 \checkmark$$

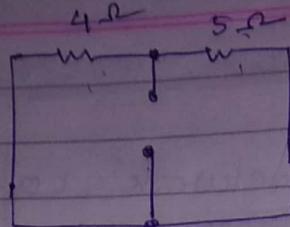

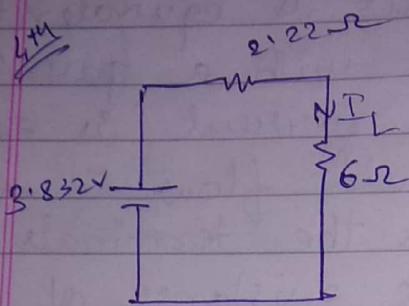
$$R_{\text{sh}} = 4 \parallel 5 = 2.22 \Omega$$



$$3.83 - 2.22I - 6I = 0$$

$$\begin{aligned} I &= \frac{3.83}{2.22} \\ &= 0.466 \text{ A} \end{aligned}$$


Norton
1st

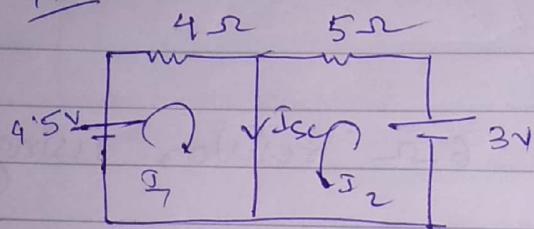

$$I_{\text{sc}} = I_1 + I_2$$


$$\begin{aligned} &= \frac{4.5}{4} + \frac{3}{5} \\ &= 1.72 \text{ A} \end{aligned}$$

2nd

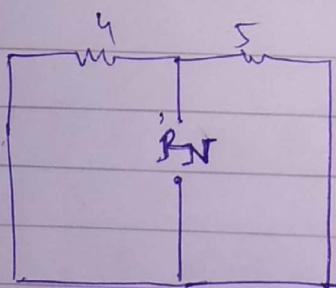

$$R_N = 5 \parallel 4 = 2.22 \Omega$$

3rd

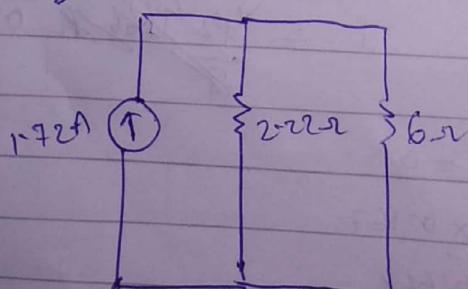


$$\begin{aligned} &\frac{2.22 \times 1.72}{6 + 2.22} \\ &= \frac{2.22}{8.22} \times 1.72 \\ &= 0.464 \end{aligned}$$

Star/Delta & Delta/Star transformations.

In some cases resistances are neither connected in series nor connected in parallel. In those cases the resistances may be connected in star or Delta.

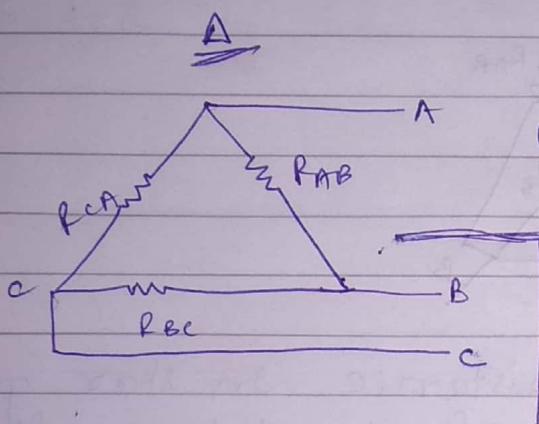so for simplification we either convert star - delta or from delta - star.



(1) Resistance b/w terminal A & B in Δ .


$$= R_{AB} + \frac{1}{2}(R_{CA} + R_{BC}) \quad \text{--- (1)}$$

$$= \frac{R_{AB} \times (R_{CA} + R_{BC})}{R_{AB} + R_{CA} + R_{BC}} \quad \text{--- (1)}$$

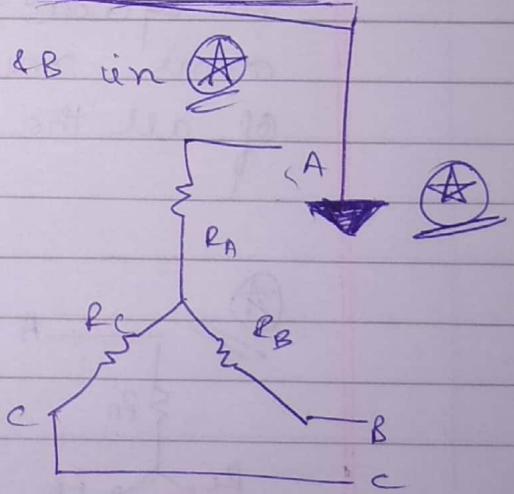(2) Resistance b/w terminal A & B in \circledast

$$= R_A + R_B \quad \text{--- (2)}$$

So; $R_A + R_B = \frac{R_{AB} \times (R_{BC} + R_{CA})}{R_{AB} + R_{BC} + R_{CA}} \quad \text{--- (3)}$



$$R_B + R_C = \frac{R_{BC} \times (R_{CA} + R_{AB})}{R_{BC} + R_{CA} + R_{AB}} \quad \text{--- (4)}$$


$$R_C + R_A = \frac{R_{CA} \times (R_{AB} + R_{BC})}{R_{AB} + R_{BC} + R_{CA}} \quad \text{--- (5)}$$

Sub eqⁿ ④ from ③ & add it to ⑤


$$R_A = \frac{R_{AB} \cdot R_{CA}}{R_{AB} + R_{BC} + R_{CA}} \quad (6)$$

$$R_B = \frac{R_{AB} \cdot R_{BC}}{R_{AB} + R_{BC} + R_{CA}} \quad (7)$$
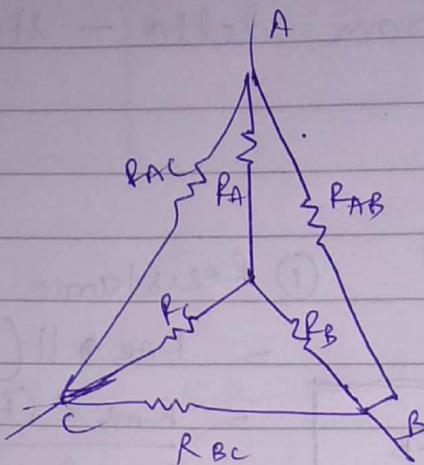
$$R_C = \frac{R_{AC} \cdot R_{BC}}{R_{AB} + R_{BC} + R_{CA}} \quad (8)$$



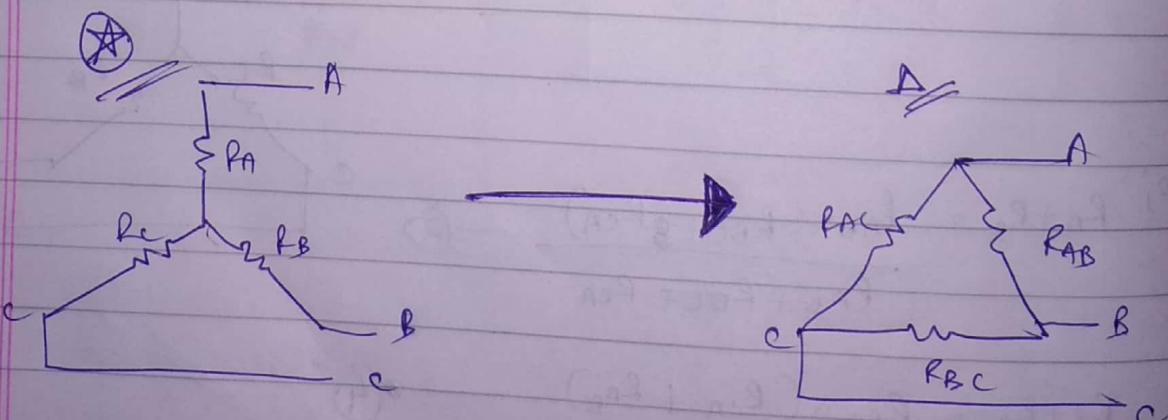∴ An arm's resistance in star pattern is equal to the product of the adjacent arm's resistance, divided by the sum of all the arm's resistances in the Δ pattern.



Dividing eqnⁿ ⑥ by ⑦



$$\frac{R_A}{R_B} = \frac{R_{CA}}{R_{BC}} \Rightarrow R_{CA} = \frac{R_A \times R_{BC}}{R_B}$$

$$\Rightarrow R_{BC} = R_B + R_C + \frac{R_B R_C}{R_A}$$



$$R_{AC} = R_A + R_C + \frac{R_A R_C}{R_B}$$

$$R_{AB} = R_A + R_B + \frac{R_A \cdot R_B}{R_C}$$

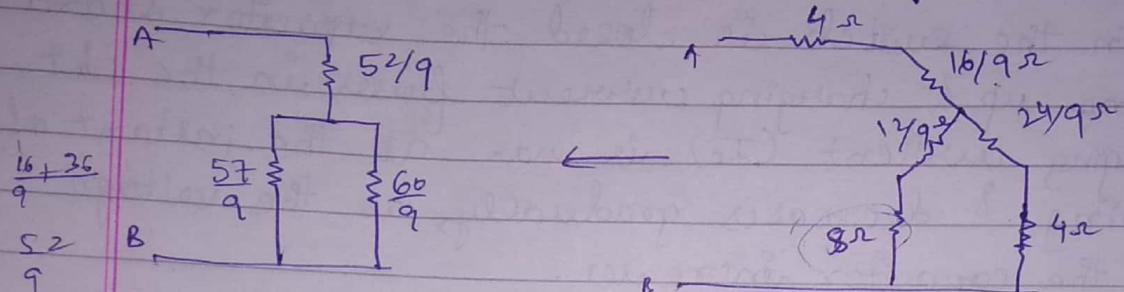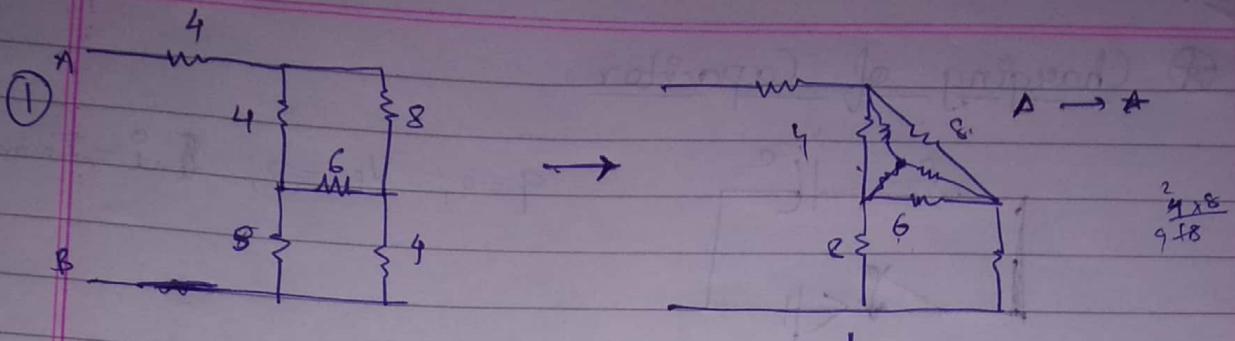\therefore  Resistance b/w 2 terminals of Δ is equal to
(sum of star resistances connected to those terminals) + (product of the same two resistances)
divided by the 3rd star resistance.


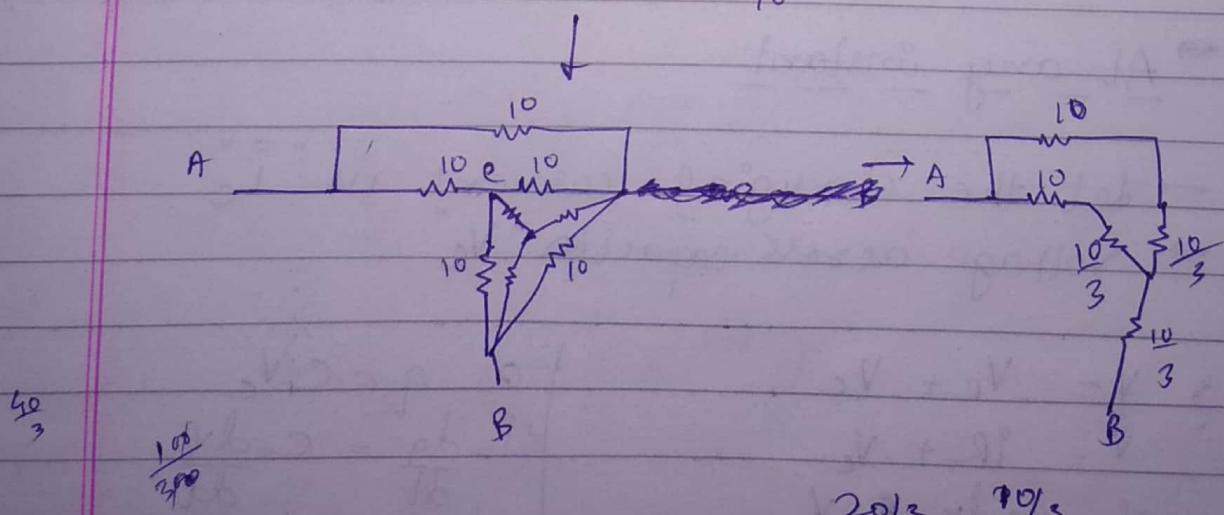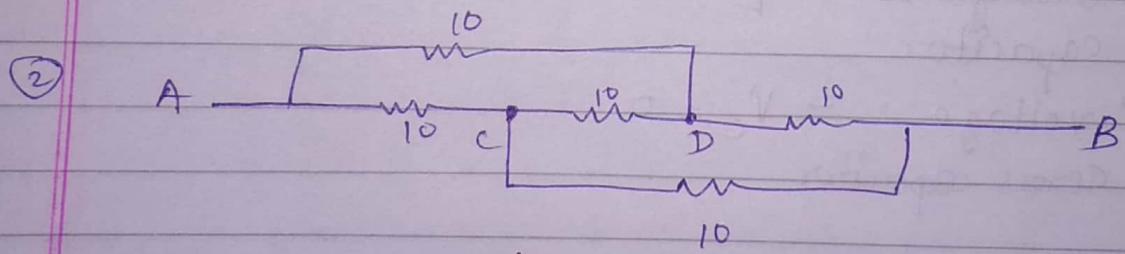
$$\begin{aligned}
 & \frac{12+8}{9} \quad \frac{72+12}{9} \quad \frac{9}{57} + \frac{9}{60} \\
 & \frac{45}{57} \quad \frac{84}{9} \quad \left(\frac{84+60}{37} \right) \\
 & \frac{12+4}{9} \quad \frac{87}{9}
 \end{aligned}$$




$$\frac{20}{3} \quad \frac{10}{3}$$

$$A - \xrightarrow{10\text{ ohm}} B$$

~~V_o = I_{max}~~

★ Charging of Capacitor

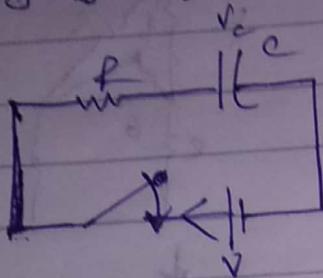

$$q=0; V_c=0; i=I_{\text{max}}$$

- ↳ When the switch is closed, the capacitor starts charging up & charging current flows in the ckt.
- ↳ Charging current (I_c) is max at the instant of switching & decreases gradually as the voltage across the capacitor increases.
- ↳ When capacitor voltage = V , $I_c = 0$

① At switching ~~instant~~

$$\rightarrow \text{current} = \text{max}^m; I_{\text{max}} = \frac{V}{R}$$

$$\rightarrow \text{charge in} = q = 0$$

• capacitor

$$\rightarrow \text{voltage, } = V_c = 0$$

across capacitor

② At any instant

→ Let the charging current is " i_c "

→ Voltage across capacitor "V_c"

$$V = V_R + V_c$$

$$V = iR + V_c$$

$$V = \frac{RC}{dt} \frac{dV_c}{dt} + V_c$$

$$V = V_c + RC \frac{dV_c}{dt}$$

as $q = CV_c$

$$4i = \frac{dq}{dt} = C \frac{dV_c}{dt}$$

$$\Rightarrow \frac{dV_c}{dt} = \frac{V - V_c}{RC}$$

$$\frac{dV_c}{V - V_c} = \frac{dt}{RC}$$

$$\int \frac{dV_c}{V_0 - V_c} = \int -\frac{dt}{RC} \quad (\text{Multiplying } (-1) \text{ on both sides & integrating})$$

$$\ln(V - V_c) = -\frac{t}{RC} + K$$

$$\text{At } t=0; V_c=0$$

$$\ln V = K$$


$$\Rightarrow \ln|V - V_c| = -\frac{t}{RC} + \ln V$$

$$\ln \left| \frac{V - V_c}{V} \right| = -\frac{t}{RC}$$

$$\frac{V - V_c}{V} = e^{-t/RC}$$

$$\boxed{V - V_c = V e^{-t/RC}}$$

$$\boxed{V_c = V(1 - e^{-t/RC})}$$

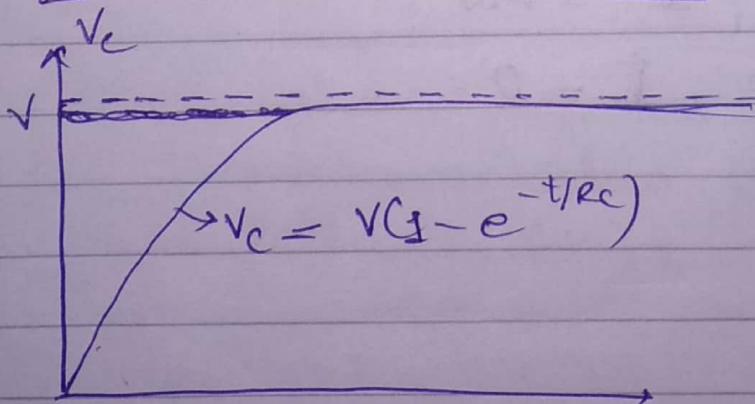

$$\& q = \sigma(1 - e^{-t/RC})$$

★ Time Constant (τ)

Time constant is the time required for the capacitor voltage to reach to 0.632 times $\approx 63.2\%$ of its steady value (or supplied voltage) = "V".

$$V_C = V(1 - e^{-t/RC})$$

$$\tau = \lambda = RC$$

$$\Rightarrow V_C = V(1 - e^{-t/\tau})$$

$$\boxed{V_C = 0.632 V}$$

★ Current in the capacitor (I_C)

$$V = V_C + IR$$

$$V - V_C = Ve^{-t/RC} = IR$$

$$\Rightarrow I = \frac{Ve^{-t/RC}}{R}$$

$$\boxed{I = I_{\max} e^{-t/RC}}$$


$$t=0; I = I_{\max}$$

$$t=\infty, I = 0.$$

★ Discharging of a Capacitor :-

$$t=0; I=I_{\max}; V_c=V$$

$$t=\infty; I=0; V_c=0$$

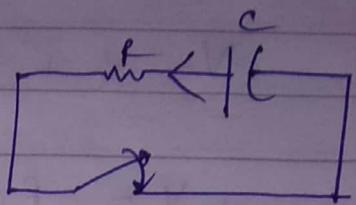

At any instant

~~$$IR + V_c = 0$$~~

$$R \frac{dV_c}{dt} = -V_c$$

~~$$\frac{dV_c}{V_c} = -\frac{dt}{RC}$$~~

$$\ln V_c = -\frac{t}{RC} + K$$

$$\text{at } t=0; V_c=V$$

$$K = \ln V$$

$$\Rightarrow \ln V_c = -\frac{t}{RC} + \ln V$$

$$\ln \frac{V_c}{V} = -\frac{t}{RC}$$

$$\boxed{V_c = V e^{-t/RC}}$$



Time constant

It is the time taken by the capacitor to discharge from maximum value to 36.7% or 0.367 of the max voltage (V).

$$t=\lambda = RC$$

$$V_c = V e^{-t/RC}$$

$$\boxed{V_c = 0.367 V}$$

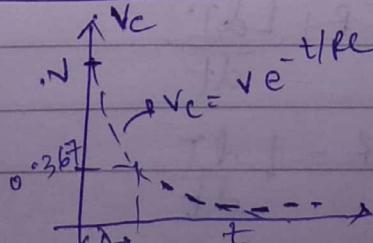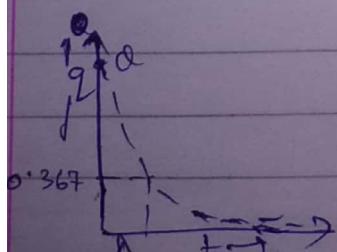

Rate of rise of voltage in the capacitor

$$V = V_c + RC \frac{dV_c}{dt}; \text{ when } i=0, V_c=0,$$

$$\Rightarrow V = RC \frac{dV_c}{dt} \Rightarrow \boxed{\frac{dV_c}{dt} = \frac{V}{RC}}$$

Closing of an inductive circuit

When the switch is closed at $t=0$, due to the presence of inductor, the current in the circuit will be zero.


$$V = V_R + V_L$$

$$V = IR + V_L$$

$$\text{If } I=0; \quad V_R=0 \\ \Rightarrow \boxed{V = V_L}$$

$$V_L = L \frac{di}{dt} = V$$

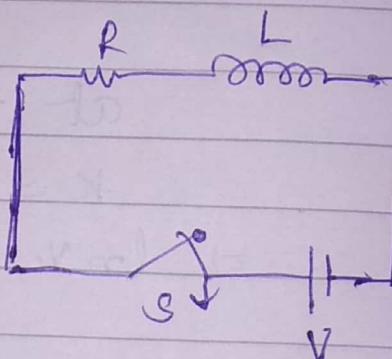\therefore as $i \uparrow$; $V_R \uparrow$; $V_L \downarrow$; $\frac{di}{dt} \downarrow$ (as $L = \text{const.}$)



Consider that the current rises from zero (0) to $I = I_{\text{max}} = \frac{V}{R}$ in a small time t .

At any instant the current is increasing at the rate $\frac{di}{dt}$

$$V = V_R + V_L$$

$$V = IR + L \frac{di}{dt}$$

$$V - IR = L \frac{di}{dt}$$

$$\Rightarrow \int \frac{dI}{V - IR} = \int \frac{dt}{L}$$

$$\Rightarrow -R \int \frac{dI}{V - IR} = -\frac{R}{L} \int dt$$

$$\Rightarrow \ln |V - IR| = -\frac{R}{L}t + K$$

\therefore as at $t=0$; $I=0$.

$$\Rightarrow \ln V = K$$

$$\Rightarrow \ln |V - IR| = -\frac{R}{L}t + \ln V$$

$$\Rightarrow \ln \left| \frac{V - IR}{V} \right| = -\frac{R}{L}t$$


$$\Rightarrow V - IR = V e^{-\frac{R}{L}t}$$

$$V - V e^{-\frac{R}{L}t} = IR$$

$$V(1 - e^{-\frac{R}{L}t}) = IR$$

$$\Rightarrow I = \frac{V}{R} (1 - e^{-\frac{R}{L}t})$$
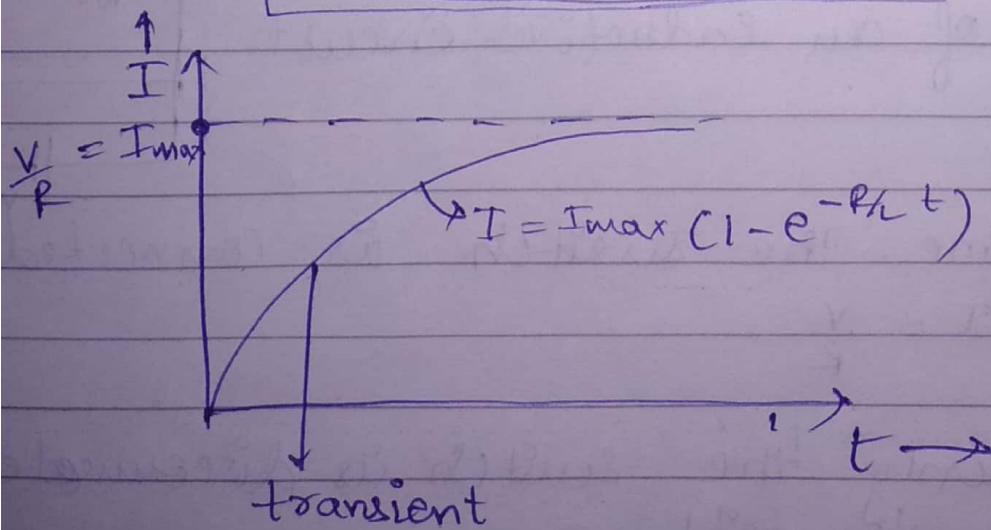
$$\Rightarrow \boxed{I = I_{max} (1 - e^{-\frac{R}{L}t})}$$



Time Constant

$$\tau = t = \frac{L}{R}$$

$$I = I_{\max} (1 - e^{-t/\tau})$$

$$\Rightarrow I = 0.632 I_{\max}$$

$\therefore \tau$ is the time taken by ~~an inductor~~ current to reach 0.632 times of its maximum or final stage value.


Initial rate of rise of current

$$V = IR + L \frac{dI}{dt}$$

$$I=0; V_R=0$$

$$V = L \frac{dI}{dt} \Rightarrow \boxed{\frac{dI}{dt} = \frac{V}{L}}$$

Breaking of an inductive circuit

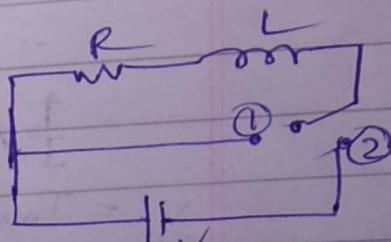

(1) A long time the switch is connected to pos 2 $\therefore I = \frac{V}{R}$.

(2) Now suddenly the switch is disconnected from posⁿ 2 to posⁿ 1.

$$IR + L \frac{dI}{dt} = 0$$

$$\Rightarrow \frac{dI}{I} = -\frac{R}{L} dt$$

$$\Rightarrow \ln I = -\frac{R}{L} t + k$$

$$^{\circ} \text{as at } t=0; I = \frac{V}{R} = I_{\max}$$

$$\Rightarrow k = \ln I_{\max}$$

$$\Rightarrow I = I_{\max} e^{-\frac{R}{L} t}$$

Time constant

$$t = \lambda = \frac{L}{R}$$

$$I = I_{\max} e^{-\frac{t}{\lambda}}$$

$$I = I_{\max} (0.37)$$

↳ If t is the time reqd. for the current to fall to (0.37) times of its initial steady value I_{\max} .

① A $2\mu F$ capacitor is connected by closing switch to a supply of $100V$ through a $1M\Omega$ series resistor.

(i) Calculate $\lambda = \frac{1}{RC} = 10^{-6}$

(ii) Initial changing current = $\frac{100}{10^6} = 10^{-4}A$

(iii) Initial rate of rise of capacitor = $\frac{100}{10^6 \times 2 \times 10^{-6}} = 50V/s$

(iv) Voltage across capacitor after 6sec
of closing switch.

$$\begin{aligned} V &= 100(1 - e^{-\frac{6}{2}}) \\ &= 100(1 - e^{-3}) \\ &= 100(1 - 0.05) \\ &= 100(0.95) \\ &= 95.1V \end{aligned}$$

② A coil having resistance of 15Ω & $L = 10H$ is connected to a constant DC $75V$ supply.

(i) Find rate of change of current at the instant of closing the switch.

$$\frac{dI}{dt} + 15I = 75 \quad \text{at } t=0, I=0$$

(ii) Final steady value = $\frac{V}{R} = 5A$

$$(iii) \lambda = \frac{L}{R} = 0.67s$$

(iv) Time taken for the current to reach a value of $4A$.

$$4 = I(1 - e^{-\frac{t}{0.67}})$$

$$I = 1.07As$$

AC - voltage

It is that voltage whose magnitude & polarity changes wst time.

AC - current

It is that current whose magnitude & polarity changes wst time.


→ A sinusoidal alternating voltage is generated by rotating a coil with a constant velocity in a uniform magnetic field.

$$e = E_m \sin \omega t = E_m \sin \theta \quad (\text{Why sine?})$$

→ (i) Sine wave ~~square~~ produce lesser copper & iron loss for a given output. \therefore Efficiency is more.

(ii) Sine waves ~~square~~ produces least disturbance in phone lines.

Generation of Alternating Voltage

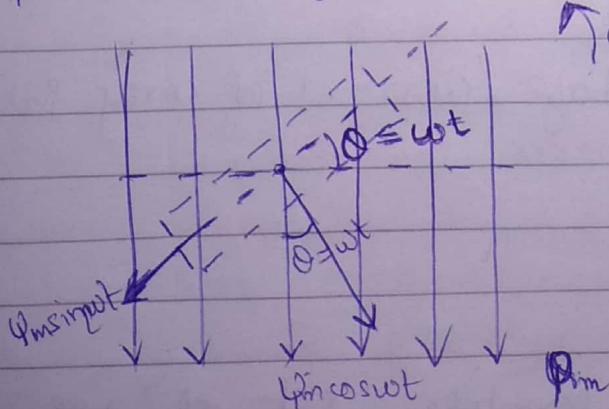

(i) Consider a rectangular coil which is rotating in an uniform magnetic field of angular velocity "w".

(ii) Alternating voltage is generated according to faraday's laws of electromagnetic induction

$$\therefore \text{Total flux linkage} = \text{No. of turns} \times \text{flux linkage}$$

$$= n \times \Phi_m \cos \omega t$$

$$\text{EMF induced} = \text{Rate of change of flux linkage}$$


$$= \frac{d}{dt} (n \Phi_m \cos \omega t)$$

$$\Rightarrow e = -n \Phi_m \omega \sin \omega t$$

$$\Rightarrow E_m = n \Phi_m \omega$$

$$\Rightarrow e = E_m \sin \omega t = E_m \sin \theta$$

★ Glossary

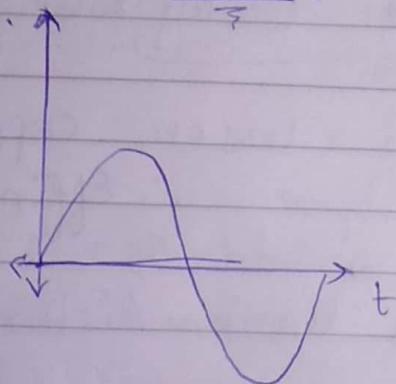

(i) Wave shape or wave form
 It is the curve obtained by taking the instantaneous values of voltage or current on ordinate against time as absciss. It is called as waveform.

(ii) Instantaneous value

The value of voltage / current of any instant is called inst. value.

(iii) * Cycle \rightarrow It is the complete set of +ve & -ve values of a particular quantity.
 1 cycle $\Rightarrow 2\pi$ radians or 360° .

(iv) Alternation

One half-cycle of an alternating quantity is called ~~of~~ alternation

(v) Time period

Time required to complete one cycle.

(vi) Amplitude

If it is the max or min value of the alternating value.

★ Different forms of an alternating quantity.

$$e = E_m \sin \omega t = E_m \sin 2\pi f t = E_m \sin \frac{2\pi}{T} t$$
$$= E_m \sin \theta$$


★ Values of an alternating quantity -

(i) Instantaneous value.

(ii) Maximum / Peak value.

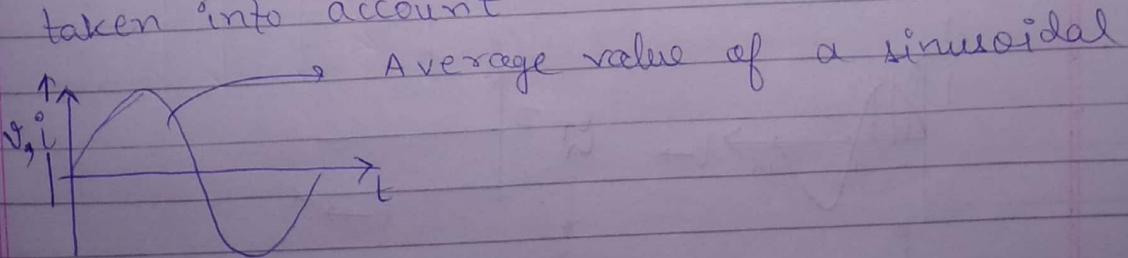(iii) Average value \rightarrow It is the arithmetical average of all the values of an alternating quantity over 1 cycle.

For symmetrical wave, since the average value is zero (over 1 cycle), average value of 1 alternation is taken into account



"Avg value of \pm half of a cycle" -

$$= \frac{\text{Area of one alternation}}{\text{Base of one alternation}}$$

$$\therefore \text{Area of 1 alternation} = \int_{\frac{\pi}{2}}^{\pi} I d\theta$$

$$= \pi \int_0^{\pi} I_m \sin \theta d\theta$$

$$= I_m [-\cos \theta]_0^{\pi}$$

$$= I_m [-\cos \pi + \cos 0]$$


$$= 2I_m$$

$$\therefore \text{Avg value of alt. current} = \frac{2I_m}{\pi} = 0.632 I_m$$

$$\& \text{Avg value of alt. voltage}$$

④ RMS value of Effective value

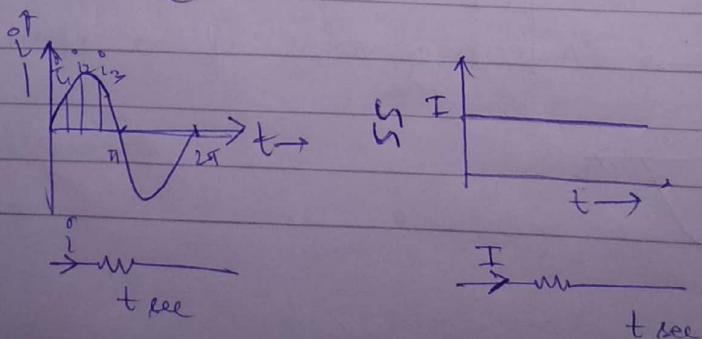It is that steady state DC value which when flowing through a given resistance for a given time produces the same amount of heat as produced by the alternating current when flowing through the same resistance for the same time.



$$i^2 R t$$

$$I^2 R t$$

$$i_1^2 R t_n + i_2^2 R t_n + i_3^2 R t_n + \dots + i_n^2 R t_n = I^2 R t$$

$$\frac{Rt}{n} (i_1^2 + i_2^2 + \dots + i_n^2) = I^2 R t$$

$$I = \sqrt{\frac{i_1^2 + i_2^2 + \dots + i_n^2}{n}}$$

↳ For symmetrical wave, RMS value can be calculated for half cycle or full cycle. But for unsymmetrical wave

★ RMS value of sinusoidal alternating quantity

$$\text{RMS value} = \sqrt{\frac{(\text{Av. of } \frac{1}{2} \text{ cycle of wave})^2}{\text{Base of } \frac{1}{2} \text{ cycle of squared wave}}}$$

∴ Av. of $\frac{1}{2}$ cycle of wave :

$$= \pi \int_0^{\pi} I_m^2 \sin^2 \omega t dt$$

$$= I_m^2 \int_0^{\pi} \left(\frac{1 - \cos 2\theta}{2} \right) d\theta$$

$$= I_m^2 \left[\frac{\theta}{2} - \frac{\sin 2\theta}{4} \right]_0^{\pi}$$

$$= I_m^2 \left[\frac{\pi}{2} - 0 \right] = \frac{\pi I_m^2}{2}$$

$$= \frac{\pi I_m^2}{2}$$

$$\therefore \text{RMS value} = \sqrt{\frac{\pi I_m^2}{2}} = \frac{I_m}{\sqrt{2}}$$

$$\Rightarrow I = 0.707 I_m$$

Note

~~(*)~~ Form factor & Peak factor

$$FF = \frac{\text{RMS value}}{\text{Avg. value}}$$

for a sinusoidal wave.

$$\text{Form factor} = \frac{0.707 I_m}{0.632 I_m} = 1.11$$

$$F.F. = 1.11$$

$$\& \text{Peak factor} = \frac{\text{Max}^m \text{ value}}{\text{RMS value}}$$

$$= \frac{I_m}{0.707 I_m} = 1.414$$

$$P.F. = 1.414$$

$$\textcircled{O} \quad I = 141.4 \sin 314t \approx A \sin \omega t$$

$$A = 141.4 \quad \& \quad \omega = 314$$

$$\bullet \textcircled{1} I_m = 141.4 \text{ A}$$

$$\textcircled{2} T = \frac{2\pi}{314} = \frac{2 \times 3.14}{314} = \frac{1}{50} = 0.02 \text{ s} \quad f = \frac{1}{T} = 50. \text{ s}^{-1} \text{ Hz}$$

\circ

\circ An alternating current of frequency 60Hz has a max. value of 120 Amp.

(i) Write down the eqⁿ for the instantaneous value.

(ii) Taking time from the instant the current is zero(0), and becoming +ve, find the instantaneous value after $\frac{1}{360}$ s.

(iii) Time taken to reach 96 Amp for the 1st time

$$\omega = 2\pi f = 2 \times 3.14 \times 60 = 376.8 \text{ rad s}^{-1}$$


$$I_m = 120$$

$$\text{(i)}: I = I_m \sin \omega t \\ = 120 \sin (376.8)t$$

$$\text{(ii)}: I = 120 \sin \left(376.8 \times \frac{1}{360} \right) = \cancel{22.96} \quad 103.9 \text{ A}$$

$$\text{(iii)}: 96 = 120 \sin (376.8 t) \\ 0.8 \cancel{53.13} = 376.8 t \\ \Rightarrow t = 0.00246 \text{ s}$$

Phase :-

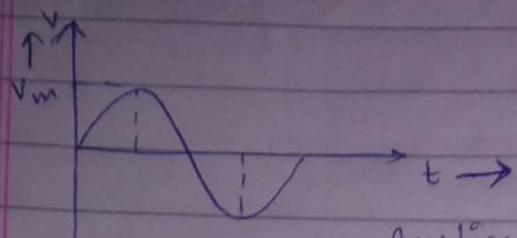

$$V = V_m \sin \omega t$$

particular
a value of

Phase of an alternating quantity is defined as the fractional part of time or cycle through which the quantity has advanced from selected zero (0) point of reference.


$$\text{When said, } V_m \sin \omega t = V_m$$

$$\sin \omega t = 1$$

$$\omega t = 90^\circ \text{ or } \frac{\pi}{2} \text{ rad}$$

$$\therefore \text{phase} = \frac{\pi}{2} \text{ rad.}$$

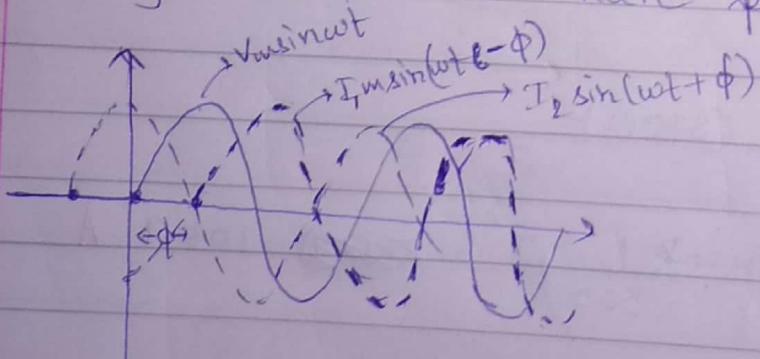When two alternating quantities having frequencies have different zero points, then they are said to have phase difference.



$$\therefore V = V_m \sin \omega t$$

$$I_1 = I_m \sin(\omega t - \phi) \rightarrow \text{lagging}$$


$$I_2 = I_m \sin(\omega t + \phi) \rightarrow \text{leading}$$

$$\text{Let } V = V_m \sin \omega t$$

$$V_R = iR = V_m \sin \omega t$$


$$\Rightarrow i = \frac{V_m \sin \omega t}{R}$$
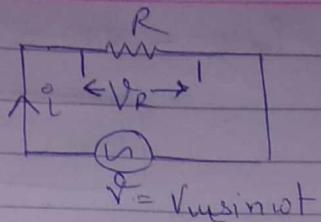
$$\Rightarrow \boxed{i = I_m \sin \omega t}$$



$$I_m = \frac{V_m}{R}$$
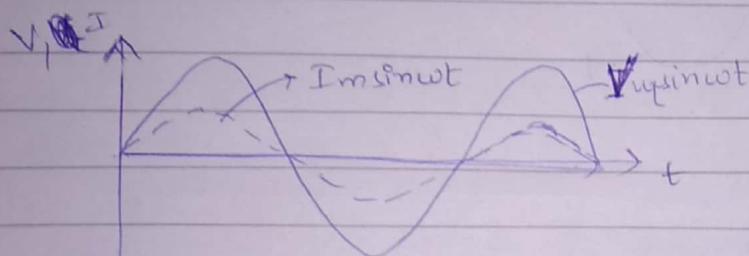
$$\Rightarrow \frac{V_m}{I_m} = \frac{\sqrt{2}V}{\sqrt{2}I} = \frac{V}{I}$$



↳ In an AC circuit, with resistance only, the applied voltage & current are in phase with each other.

Instantaneous Power (P)

~~$$P = V \cdot i$$~~

$$= V_m I_m \sin^2 \omega t$$

$$= V_m I_m \left(\frac{1 - \cos 2\omega t}{2} \right)$$


$$\therefore P_{avg} = \frac{1}{2\pi} \int_0^{2\pi} P dt$$

$$= \frac{1}{2\pi} \int_0^{2\pi} \frac{V_m I_m}{2} - \frac{V_m I_m}{2} \cos 2\omega t dt$$

$$= \frac{V_m I_m}{2} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} = \frac{V_o I}{2}$$


$$P_{avg} = VI = IRI$$

$$\boxed{P_{avg} = I^2 R}$$

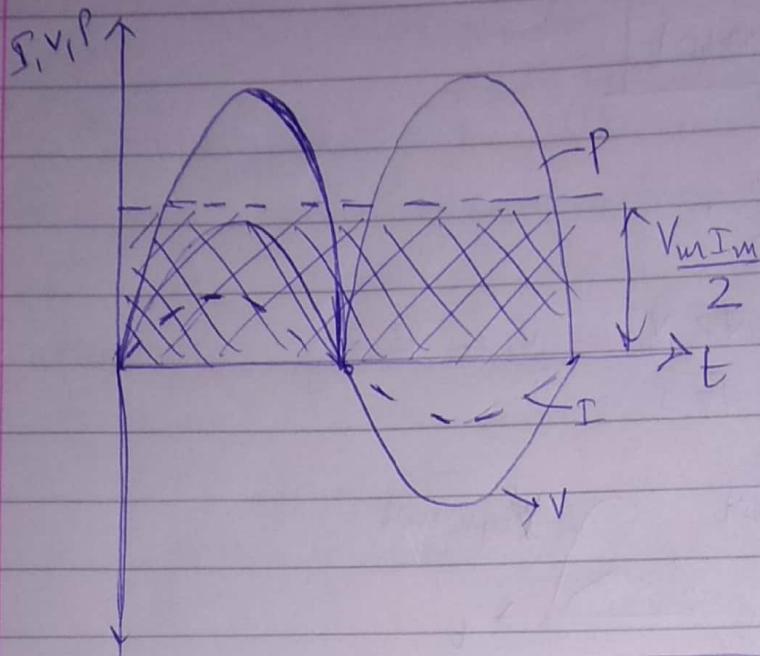

AC with Inductance

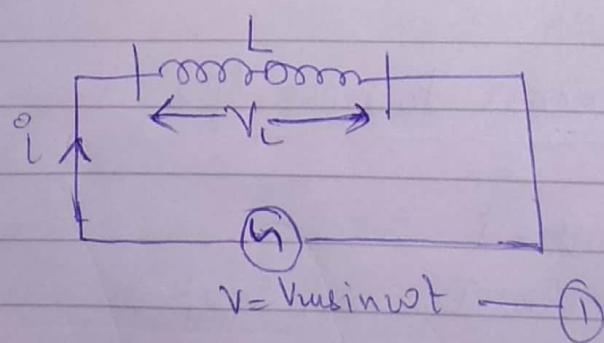When an inductor is connected across an AC supply, an EMF is induced called as Back-EMF.



$$\Rightarrow V = L \frac{di}{dt}$$

$$V_m \sin \omega t = L \frac{di}{dt}$$

$$\therefore \frac{di}{dt} = \frac{V_m \sin \omega t}{L}$$

$$\Rightarrow \int dI = \frac{V_m}{L} \int_0^t \sin(\omega t + \phi) dt$$

$$\Rightarrow I = \frac{V_m}{\omega L} (-\cos \omega t)$$

$$= \frac{V_m}{\omega L} \sin\left(\frac{\pi}{2}\omega t - \frac{\pi}{2}\right)$$

$$i = I_m \sin(\omega t - \frac{\pi}{2}) \quad \boxed{②}$$

\therefore Current of an inductor lags behind voltage by $\frac{\pi}{2}$ rad or 90° .

★ Inductive Reactance (X_L)

$$I_m = \frac{V_m}{\omega L} \Rightarrow V_m = \omega L = 2\pi f L = X_L$$

\hookrightarrow Opposition offered to the flow of current is called inductive reactance.

★ Instantaneous Power

$$P = VI$$


$$= V_m \sin \omega t \cdot I_m \sin(\omega t - \frac{\pi}{2})$$

$$= V_m I_m (\sin \omega t)(-\cos \omega t)$$

$$= -\frac{V_m I_m}{2} \sin 2\omega t$$

$$\therefore P_{avg} = \frac{1}{2\pi} \int_0^{2\pi} P dt = -\frac{V_m I_m}{4\pi} \int_0^{2\pi} \sin 2\omega t dt = 0$$

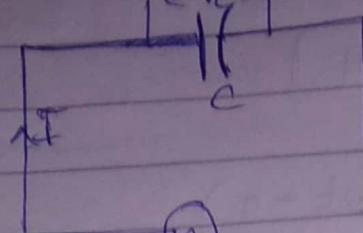NOTE Power consumed by a pure inductor is zero.



$$v = V_m \sin \omega t$$

In an AC-circuit with inductance only, the applied voltage leads the current or current lags the voltage exactly by an angle of $\pi/2$ rad or 90° .

$$V = V_m \sin \omega t$$

$$I = \frac{d\phi}{dt} = \frac{d(Vt)}{dt} = C \frac{dv_c}{dt} = C \frac{d(V_m \sin \omega t)}{dt}$$

$$= CV_m \omega \cos \omega t$$


$$= CV_m \omega \cos \omega t$$

$$\Rightarrow I = I_m \cos \omega t$$

or

$$= I_m \sin(\omega t + \pi/2)$$
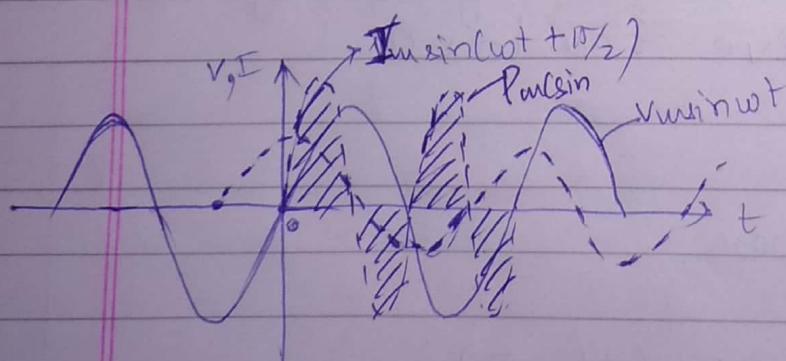
$$\therefore I = I_m \sin(\omega t + \pi/2)$$




* Capacitive Reactance

$$I_m = CV_m \omega$$

$$\frac{V_m}{I_m} = \frac{1}{\omega C} = X_C$$
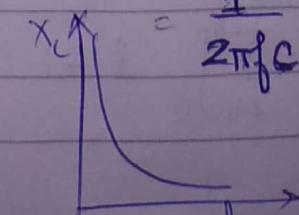
$$\therefore X_C = \frac{1}{\omega C} \Rightarrow \text{Capacitive reactance}$$



★ Instantaneous Power

$$P = \sqrt{I}$$

$$= V_m \sin \omega t \cdot I_m \sin(\omega t + \pi/2)$$

$$= V_m \sin \omega t \cdot I_m \cos \omega t$$

$$= \frac{V_m I_m}{2} (\sin 2\omega t)$$

$$\therefore P_{avg} = \frac{1}{2\pi} \int_0^{2\pi} P dt = \frac{1}{2\pi} \int_0^{2\pi} \frac{V_m I_m}{2} \sin 2\omega t dt$$

$$= \frac{V_m I_m}{4\pi} \int_0^{2\pi} \sin 2\omega t dt$$

$P_{avg} = 0$

NOTE

→ In an AC-circuit with capacitance only the applied voltage lags the current \Rightarrow the current leads the voltage by exactly $\pi/2$ or 90° .

